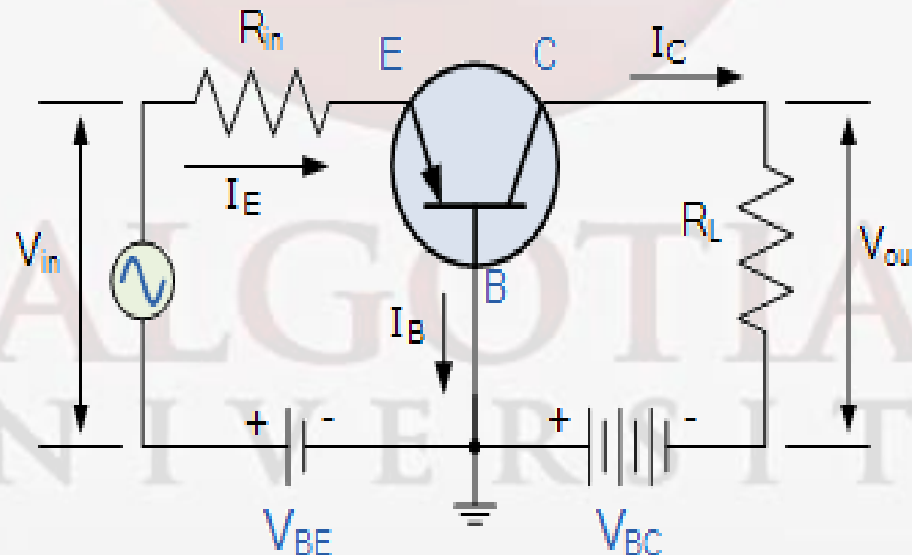


Bipolar Transistor Configurations

- ❖ As the **Bipolar Transistor** is a three terminal device, there are basically three possible ways to connect it within an electronic circuit with one terminal being common to both the input and output.
- ❖ Each method of connection responding differently to its input signal within a circuit as the static characteristics of the transistor vary with each circuit arrangement.
- **Common Base Configuration** – has Voltage Gain but no Current Gain.
- **Common Emitter Configuration** – has both Current and Voltage Gain.
- **Common Collector Configuration**—has Current Gain but no Voltage Gain.

The Common Base (CB) Configuration

- ❖ As its name suggests the **BASE connection** is common to both the input signal AND the output signal.
- ❖ The **input signal** is applied between the transistors **base and the emitter** terminals, while the corresponding **output signal** is taken from between the **base and the collector** terminals as shown




Common Base Voltage Gain

$$A_V = \frac{V_{out}}{V_{in}} = \frac{I_C \times R_L}{I_E \times R_{IN}}$$

Where: I_C/I_E is the current gain, $\alpha(\alpha)$ and R_L/R_{IN} is the resistance gain

The Common Emitter (CE) Configuration

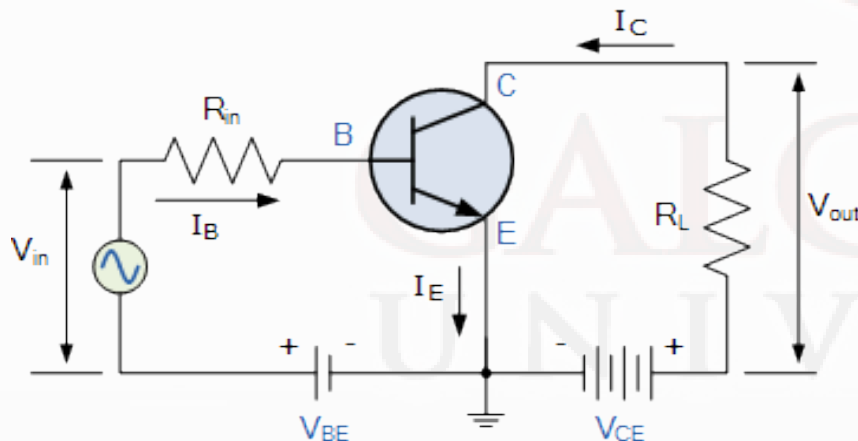- ❖ In the **Common Emitter** or grounded emitter configuration, the input signal is applied between the base and the emitter, while the output is taken from between the collector and the emitter as shown



The **common emitter amplifier** configuration produces the highest current and power gain of all the three bipolar transistor configurations. This is mainly because the **input impedance is LOW**

Course Code : BEE01T1003

Course Name:

- ❖ the **current gain** of the **common emitter transistor** configuration is quite large as it is the ratio of I_C/I_B . A transistor's current gain is given the Greek symbol of **Beta, (β)**.
- ❖ By combining the expressions for both **Alpha, α and Beta, β** the mathematical relationship between these parameters and therefore the current gain of the transistor can be given as:


$$\text{Alpha, } (\alpha) = \frac{I_C}{I_E} \quad \text{and} \quad \text{Beta, } (\beta) = \frac{I_C}{I_B}$$

$$\therefore I_C = \alpha \cdot I_E = \beta \cdot I_B$$

$$\text{as: } \alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha} \quad I_E = I_C + I_B$$

Input characteristics

- ❖ The **input characteristics** describe the relationship between input current or **base current (I_B)** and input voltage or **base-emitter voltage (V_{BE})**.
- ❖ To determine the **input characteristics**, the output voltage V_{CE} is kept constant at zero volts and the input voltage V_{BE} is increased from zero volts to different voltage levels. For each voltage level of input voltage (V_{BE}), the corresponding input current (I_B) is recorded.

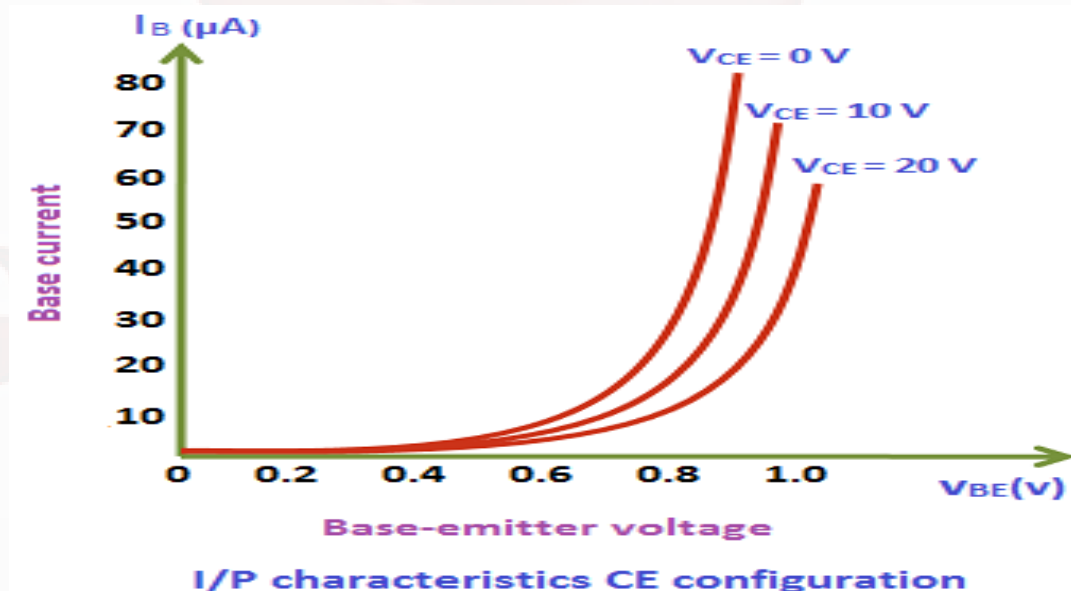

Course Code: BEEET1003

Course Name:


- ❖ A curve is then drawn between input current I_B and input voltage V_{BE} at constant output voltage V_{CE} (0 volts).
- ❖ Next, the output voltage (V_{CE}) is increased from zero volts to certain voltage level (10 volts) and the output voltage (V_{CE}) is kept constant at 10 volts. While increasing the output voltage (V_{CE}), the input voltage (V_{BE}) is kept constant at zero volts. After we kept the output voltage (V_{CE}) constant at 10 volts, the input voltage V_{BE} is increased from zero volts to different voltage levels. For each voltage level of input voltage (V_{BE}), the corresponding input current (I_B) is recorded.
- ❖ This process is repeated for higher fixed values of output voltage (V_{CE}).

Course Code: BEE01T1003

Course Name:

Output characteristics

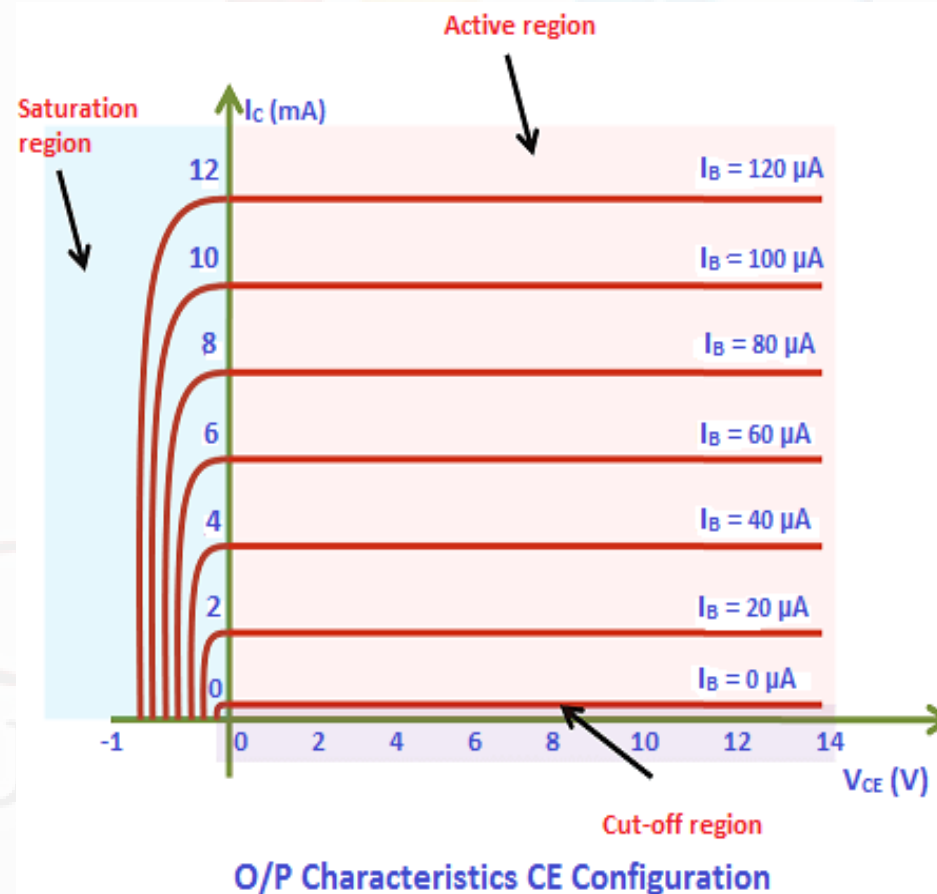- ❖ The **output characteristics** describe the relationship between **output current (I_C)** and **output voltage (V_{CE})**




Course Code: BEE01T1003

Course Name: BEEE

- ❖ A curve is then drawn between output current I_C and output voltage V_{CE} at constant input current I_B ($0 \mu A$).
- ❖ When the base current or input current $I_B = 0 \mu A$, the transistor operates in the cut-off region. In this region, both junctions are reverse biased.
- ❖ Next, the input current (I_B) is increased from $0 \mu A$ to $20 \mu A$ by adjusting the input voltage (V_{BE}). The input current (I_B) is kept constant at $20 \mu A$.
- ❖ After we kept the input current (I_B) constant at $20 \mu A$, the output voltage (V_{CE}) is increased from zero volts to different voltage levels. For each voltage level of output voltage (V_{CE}), the corresponding output current (I_C) is recorded.
- ❖ A curve is then drawn between output current I_C and output voltage V_{CE} at constant input current I_B ($20 \mu A$). This region is known as the active region of a transistor.

The Common Collector (CC) Configuration

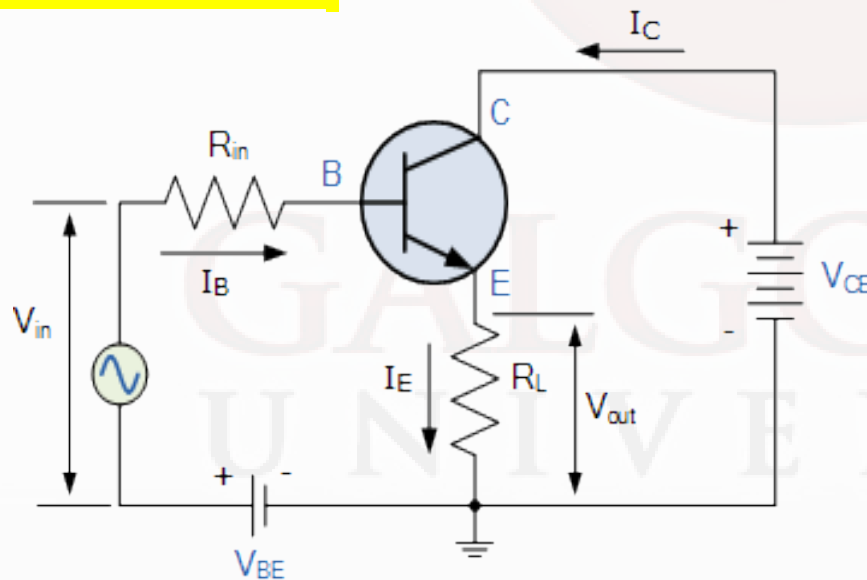- ❖ In the **Common Collector** or grounded collector configuration, the collector is connected to ground through the supply, thus the collector terminal is common to both the input and the output
- ❖ This type of configuration is commonly known as a **Voltage Follower or Emitter Follower circuit**



The Common Collector Current Gain

$$I_E = I_C + I_B$$

$$A_i = \frac{I_E}{I_B} = \frac{I_C + I_B}{I_B}$$

$$A_i = \frac{I_C}{I_B} + 1$$

$$A_i = \beta + 1$$

Course Code : BEE01T1003

Course Name:

Relationship between DC Currents and Gains

$$I_E = I_B + I_C$$

$$\alpha = \frac{I_C}{I_E} = \frac{\beta}{1 + \beta}$$

$$I_C = I_E - I_B$$

$$I_B = I_E - I_C$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{1 + \beta} = I_E (1 - \alpha) \quad I_C = \beta \cdot I_B = \alpha \cdot I_E \quad I_E = \frac{I_C}{\alpha} = I_B (1 + \beta)$$

GALGOTIAS
UNIVERSITY

L I F E

W O R K

